



POWER AMPLIFIER AND COIL DESIGN OPTIMIZATION FOR LARGE AIR GAP APPLICATIONS

TIEFENG SHI



**AIRFUEL ALLIANCE DEVELOPERS FORUM
MARCH 12-13, 2019 SHENZHEN CHINA**

- WPT and WPT Applications
 - WPT Trends and Technology Drivers
 - Wireless Power System
- High efficiency PA for WPT with GaN Systems devices
 - PA topologies
 - Constant Current Power Amplifier
 - 50W/100W/300W/1000W Class EF2 PA design
- 50W WPT system with 200mm Gap
 - Coil design for large gap
 - Topology/Requirement/Performance
 - Coil coupling distance
 - 50W 200mm system test

Everything.

Applications for Cutting the Cord

- Laptops
- Phones
- Power Tools
- eBikes
- Scooters
- Drones
- Robots (AGV)
- IP Camera
- Home appliances





30W



65W



180W



1000 to
2500W



6000 to
22000W

Trends


- Fast charge, spatial freedom, variable Tx/Rx spacing, increasing power

Technology Drivers

- High switching frequency, high current, high voltage



Source - Transmitter (Tx)

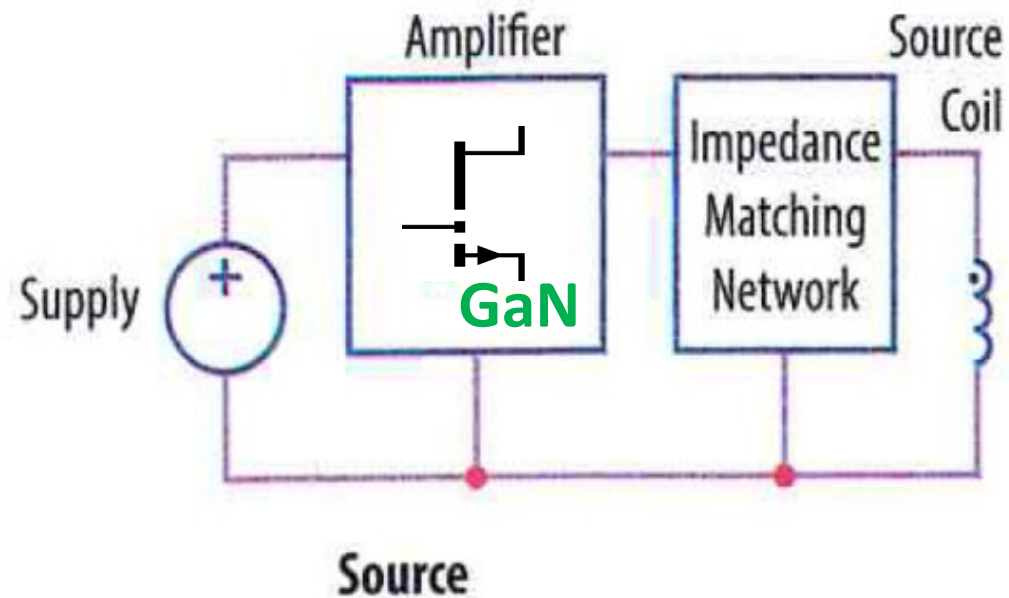1. Amplifier
2. Impedance Matching Network
3. Tx Coil



Device - Receiver (Rx)

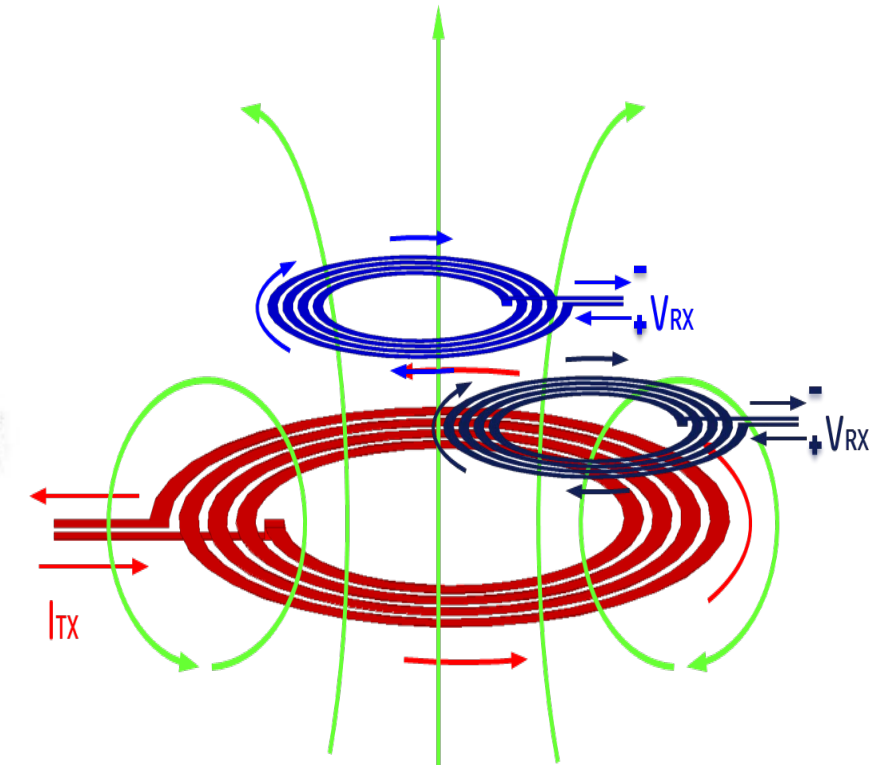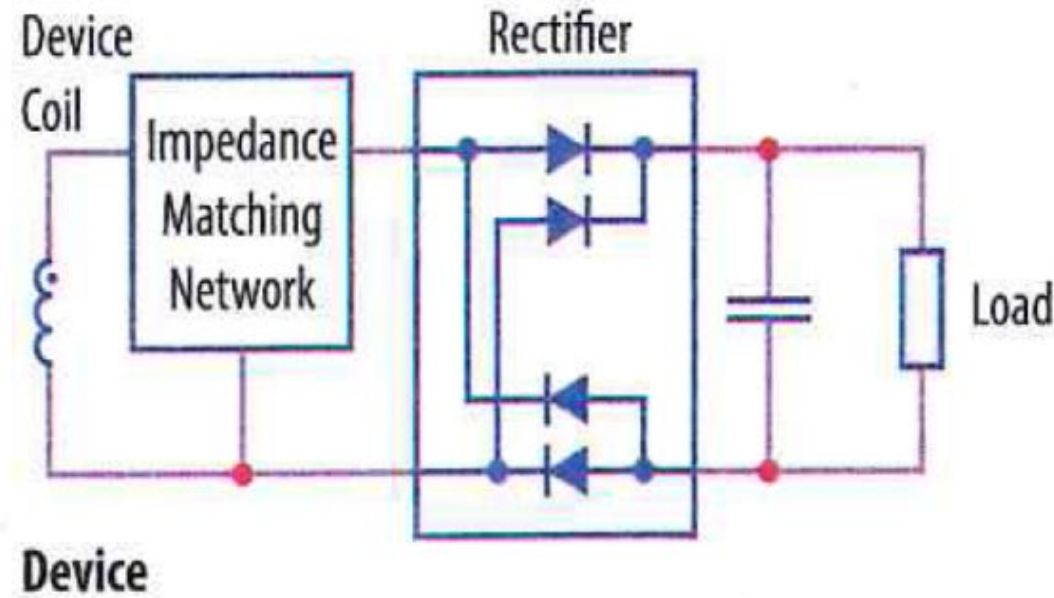1. Rx Coil
2. Impedance Matching Network
3. Rectifier




GaN FETs are used in the Transmitter Amplifier

Class D/E/EF2 topologies

Class D with ZVS

$$P = \frac{8}{\pi^2} \frac{V_R^2}{R_L} = \frac{8}{\pi^2} \frac{R_L}{(R_L + r_{\text{sat}})^2} V_{\text{cc}}^2.$$

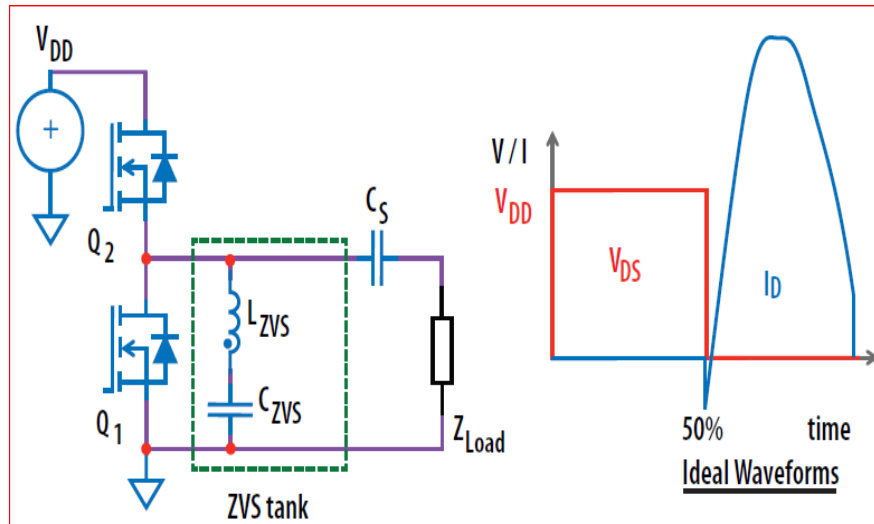
$$\eta = \frac{P}{P_0} = \frac{8}{\pi^2} \cong 81\%.$$



Class E with shunt C

$$R = \frac{8}{\pi^2 + 4} \frac{V_{\text{cc}}^2}{P_{\text{out}}} = 0.5768 \frac{V_{\text{cc}}^2}{P_{\text{out}}}.$$

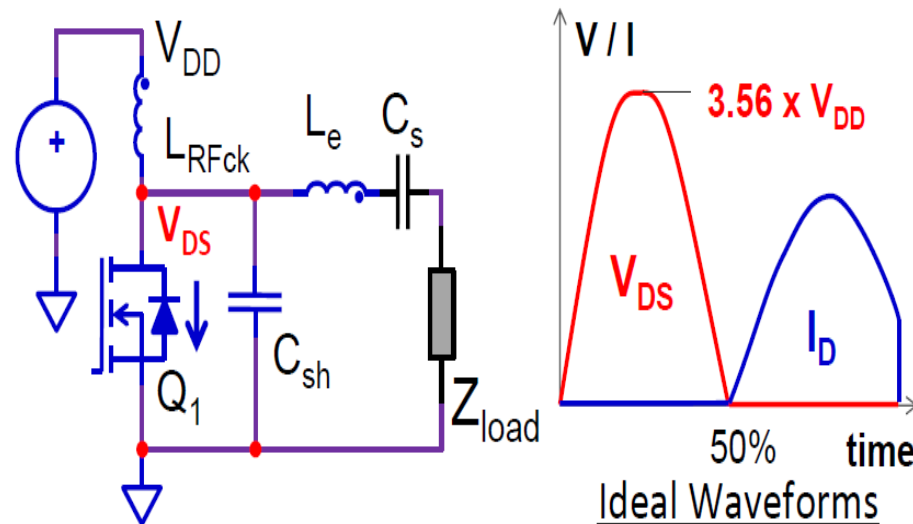
$$\eta = \frac{P_{\text{out}}}{P_0} = \frac{P_0 - P_{\text{sat}}}{P_0} = 1 - \frac{P_{\text{sat}}}{P_0}.$$



Class EF2


$$P_o = 0.6105 \frac{V_{\text{IN}}^2}{R_L}.$$
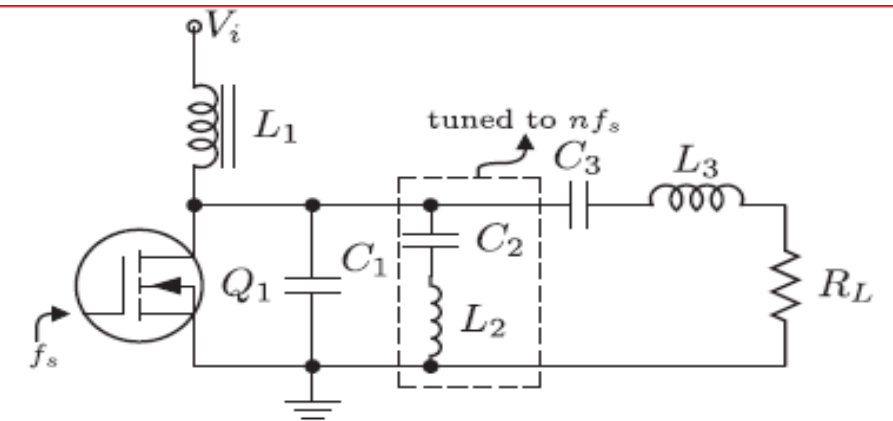
$$\eta = \frac{1}{1 + P_{L_1} + P_{\text{DS}} + P_{C_1} + P_{L_2 C_2} + P_{L_3 C_3} + P_{t_f}}.$$




Circuit diagram of the Class EF or Class E/F inverter.

“SW engineer’s solution”

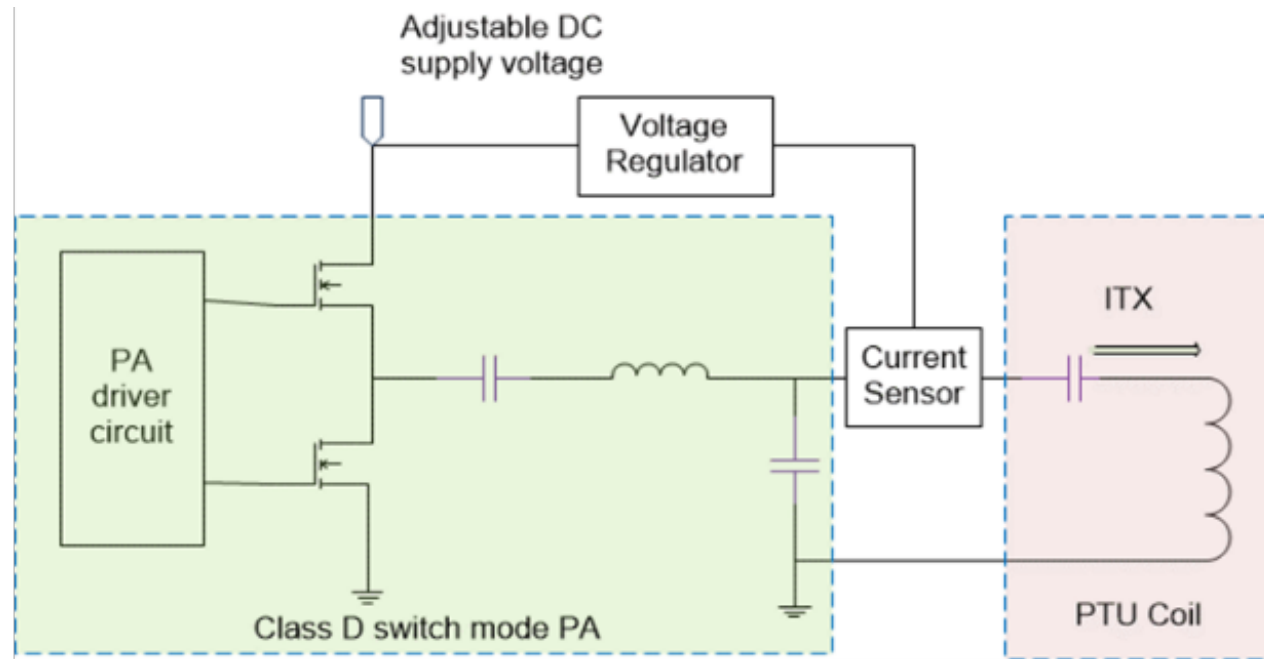

Constant Current through Feed back Control
Slow response time, poor transient handling


“RF engineer’s solution”

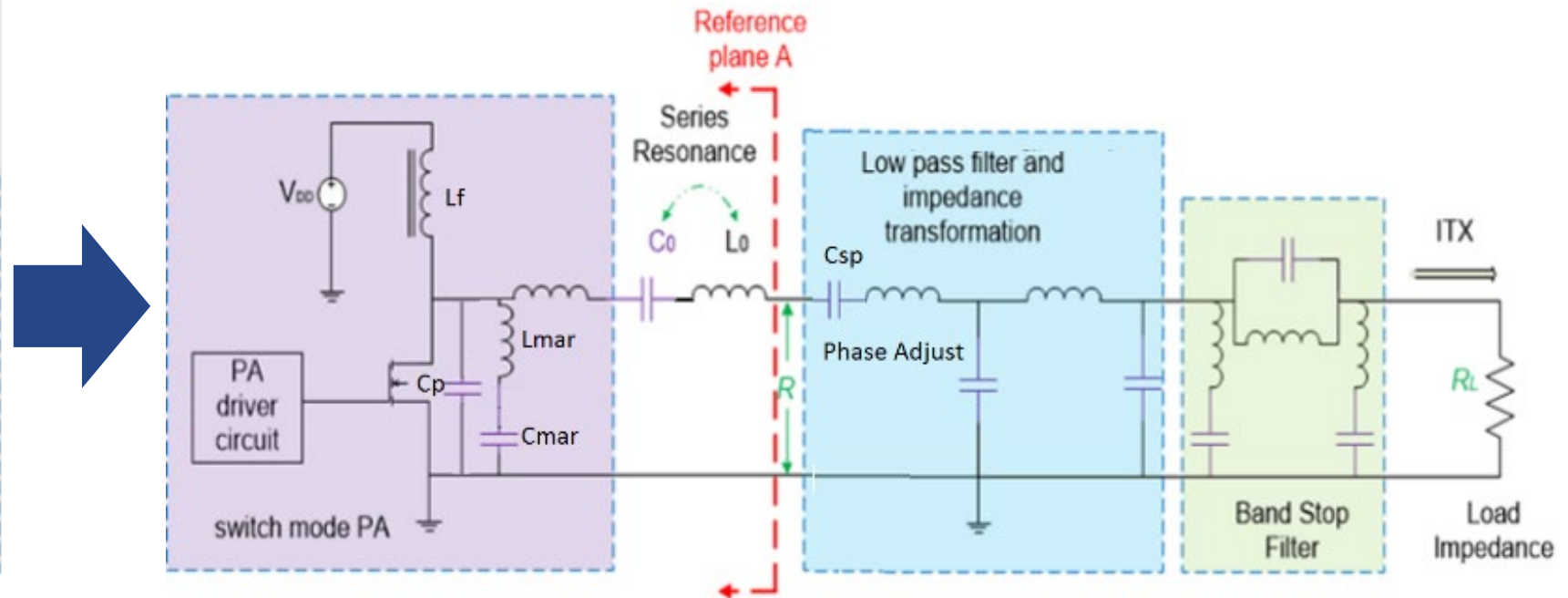


Unique output filter network designed to naturally provide constant current w/o SW feedback

“Constant Current” design methodology developed to simultaneously achieve power, efficiency, EMI and constant current behavior.


50 Watt

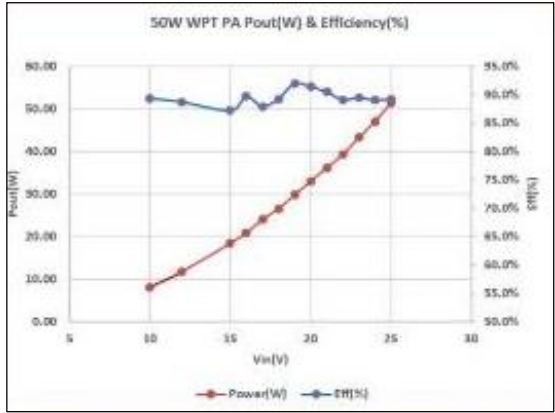


100 Watt

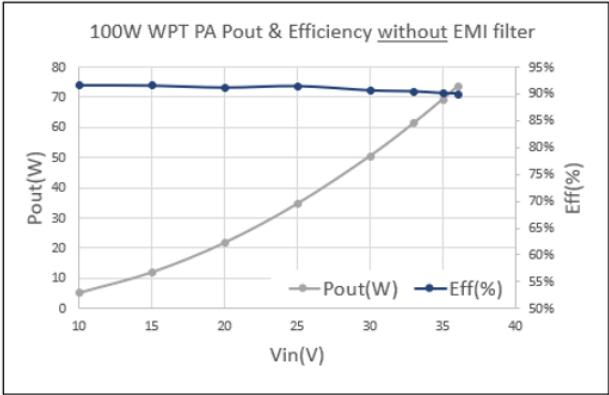


300 Watt

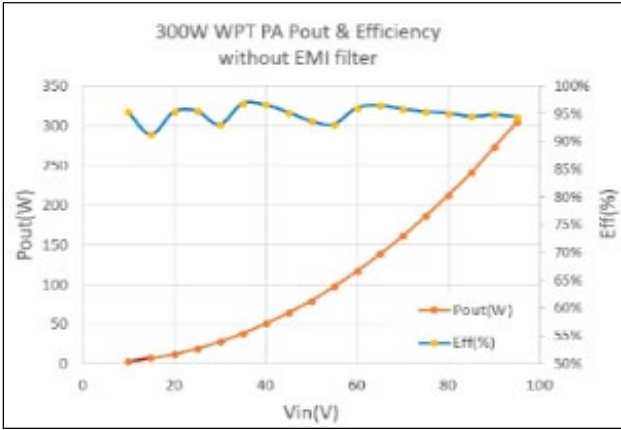

1000 Watt

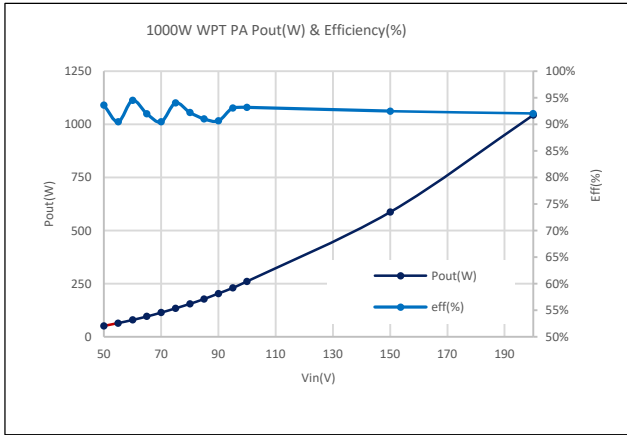

50W PA
w/GS61004B

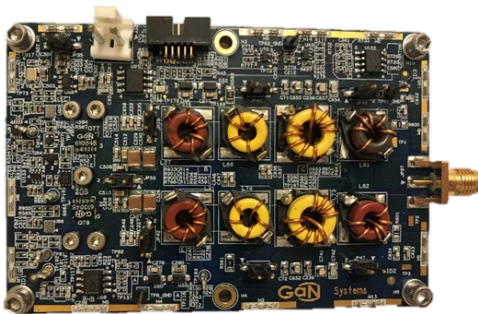


100W PA w/GS61008B







300W PA
w/GS66508B





1000W PA
w/GS66508B

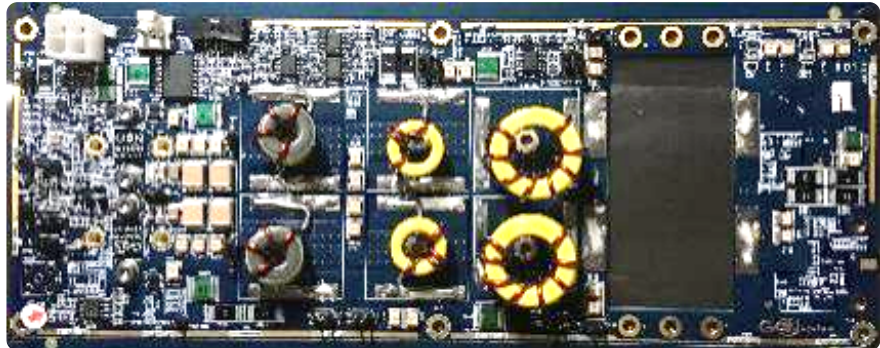

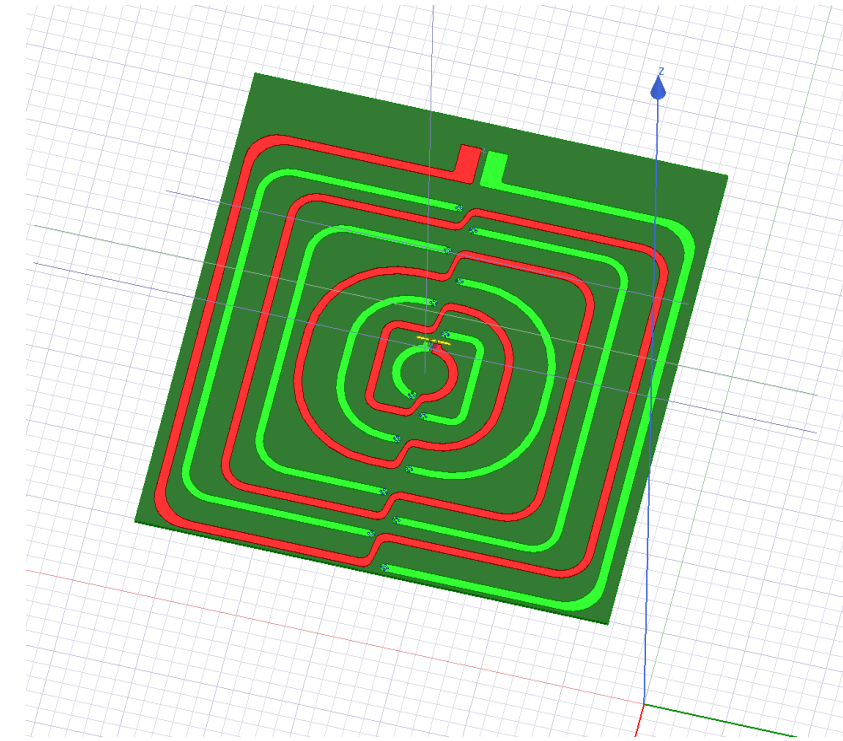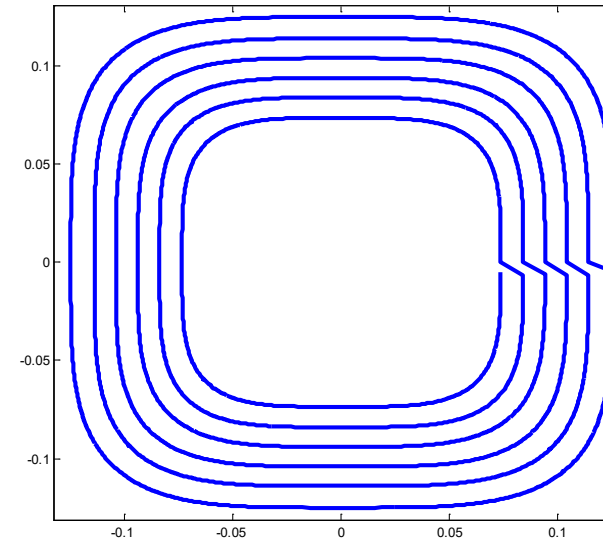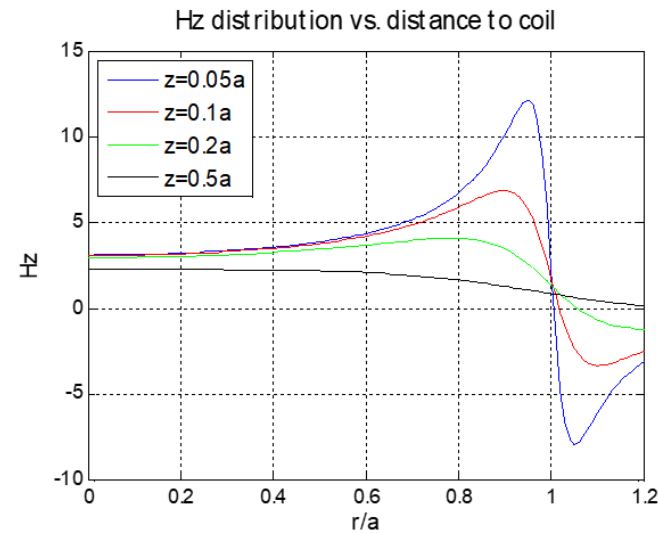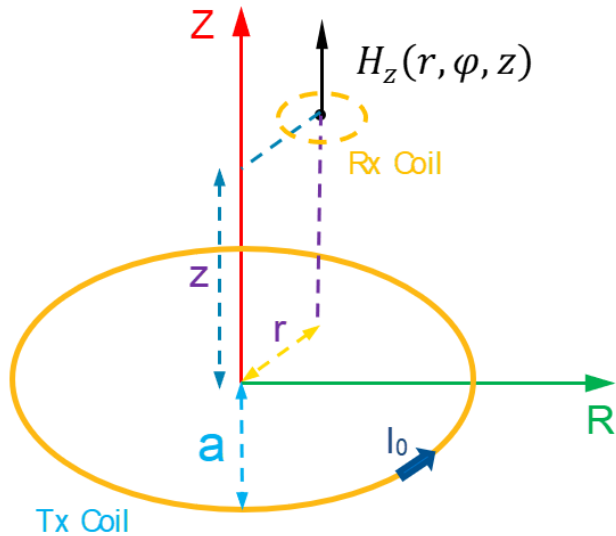

- Optimized uniform magnetic field distribution in the target area for small gap design

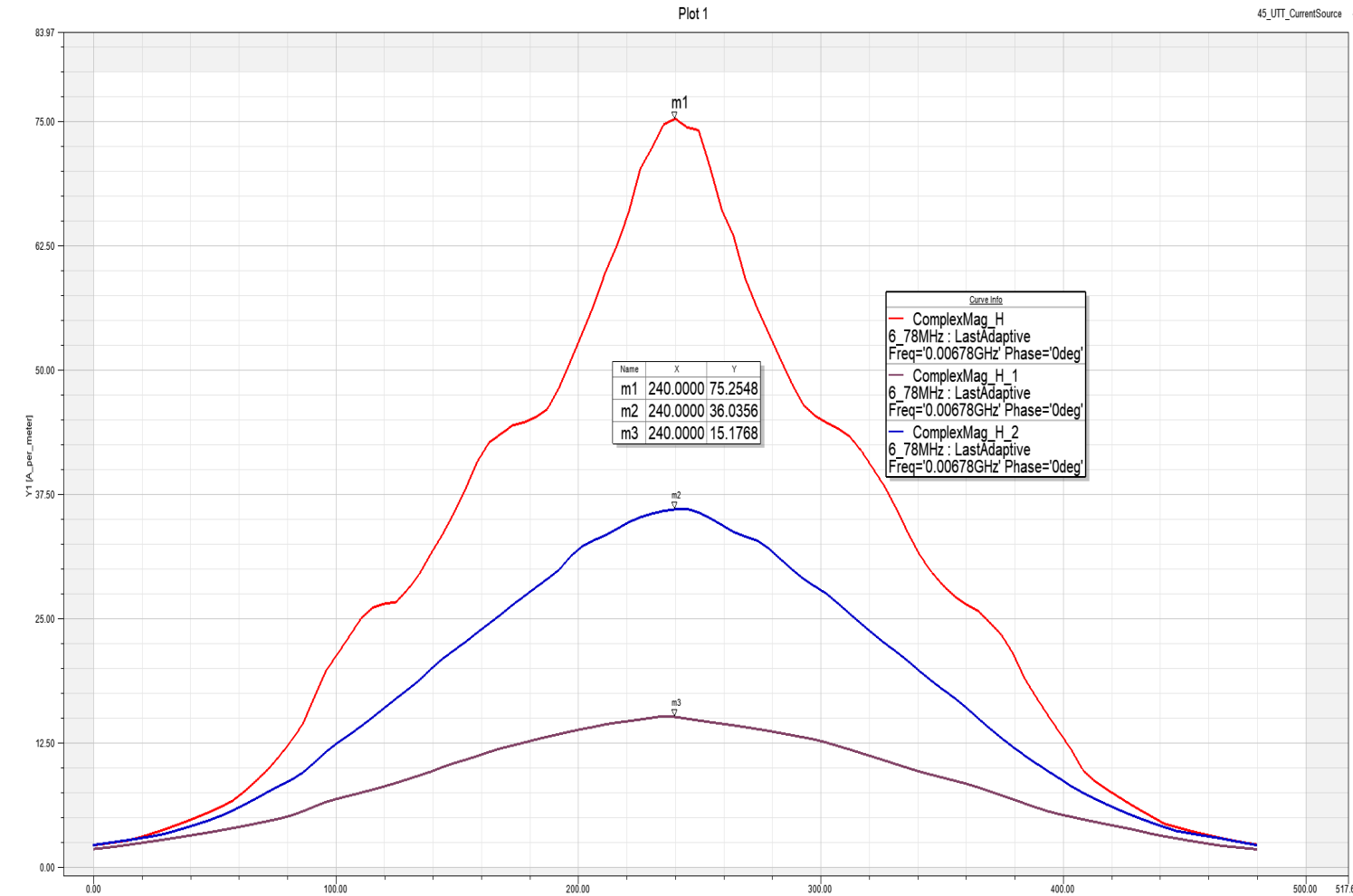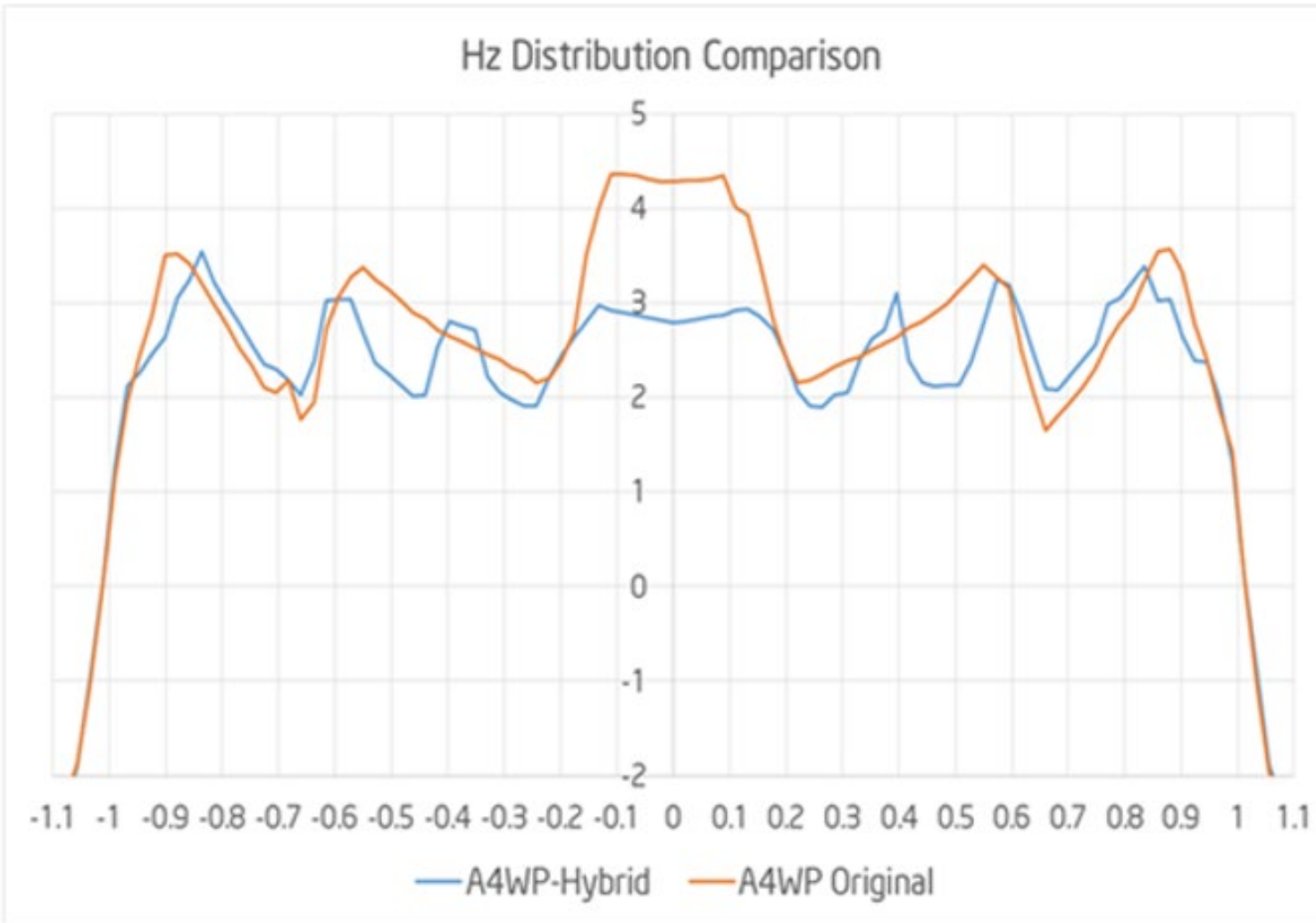
- Optimized high mutual coupling magnetic field distribution in the target area for large gap design




Uniform magnetic field distribution simulation in the target area for small, 25mm gap, design

High mutual coupling magnetic field distribution simulation in the target area for large gap design at 50, 100, 150mm height position

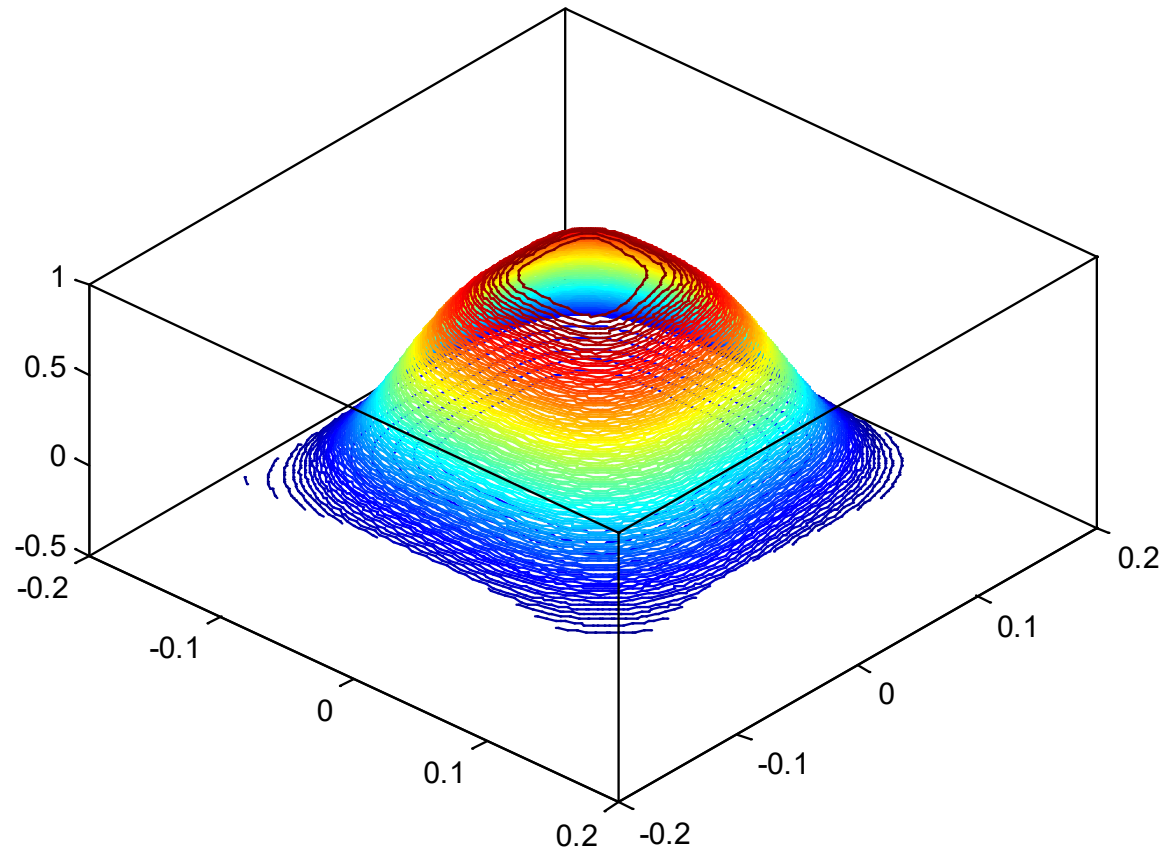Synthesize coil design with software for arbitrary size/shape for large gap coils



Small gap coil distribution

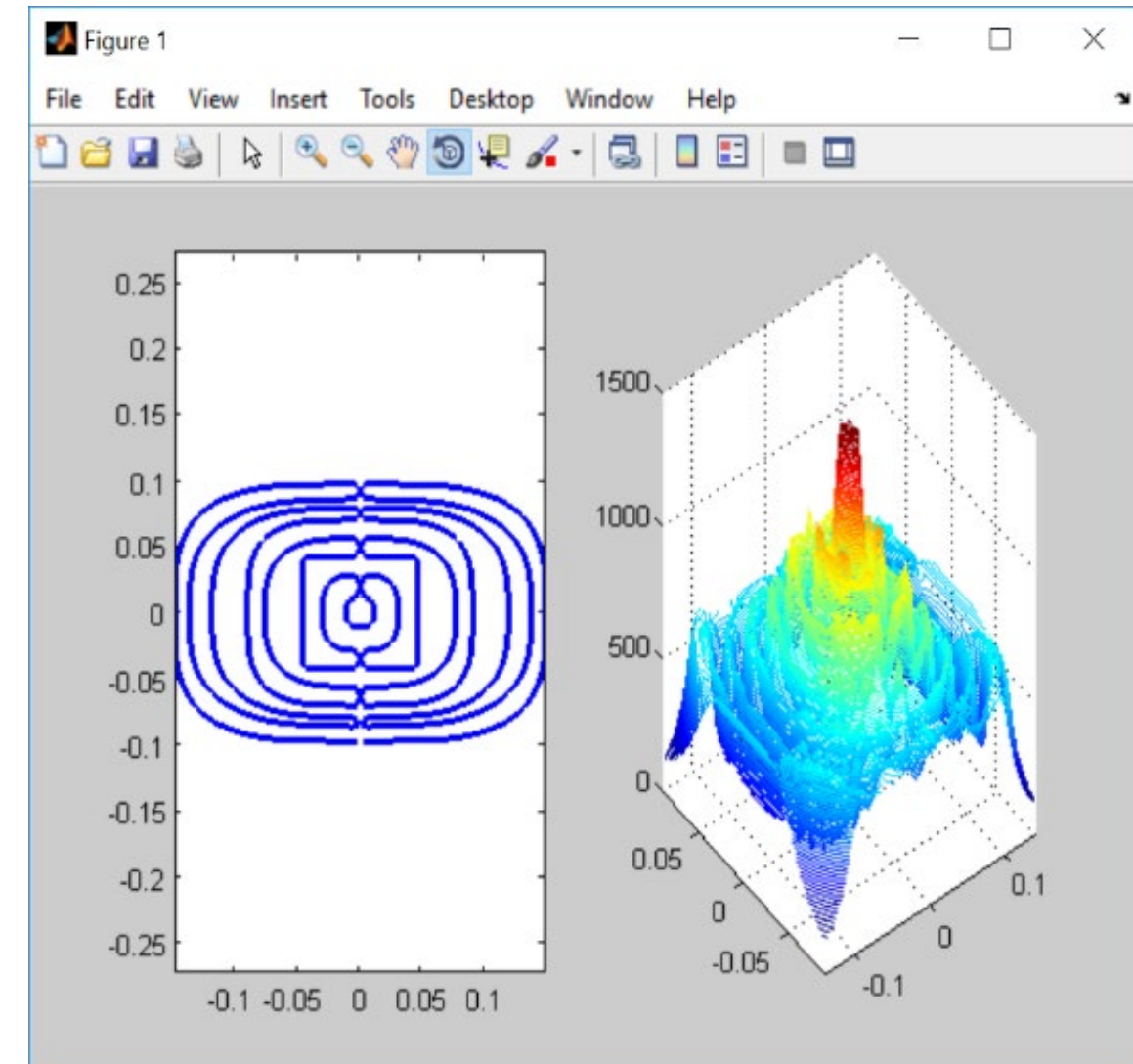


Large gap coil distribution

Coil to Coil Gap - 200 mm



Through wall demo platform


Tx coil temperature at 50W

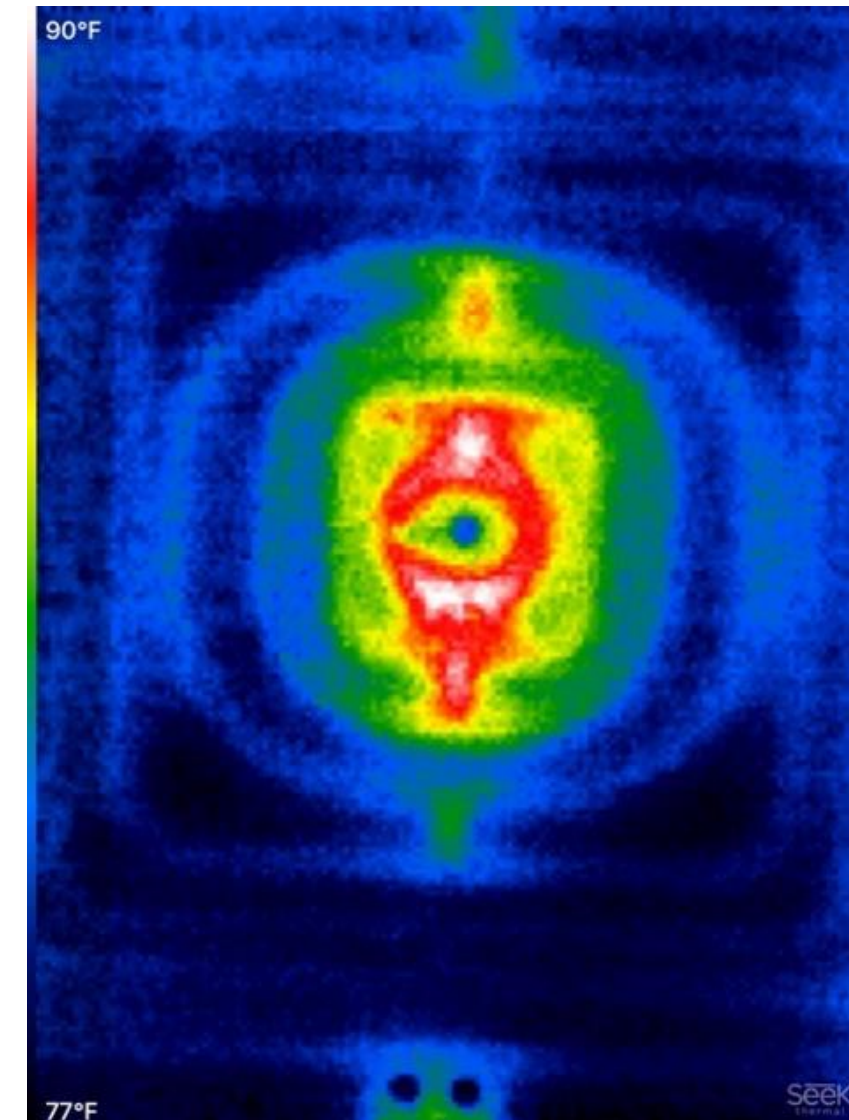

Acceptable temperature rise

50W & 100W PA SYSTEM WITH 200mm GAP

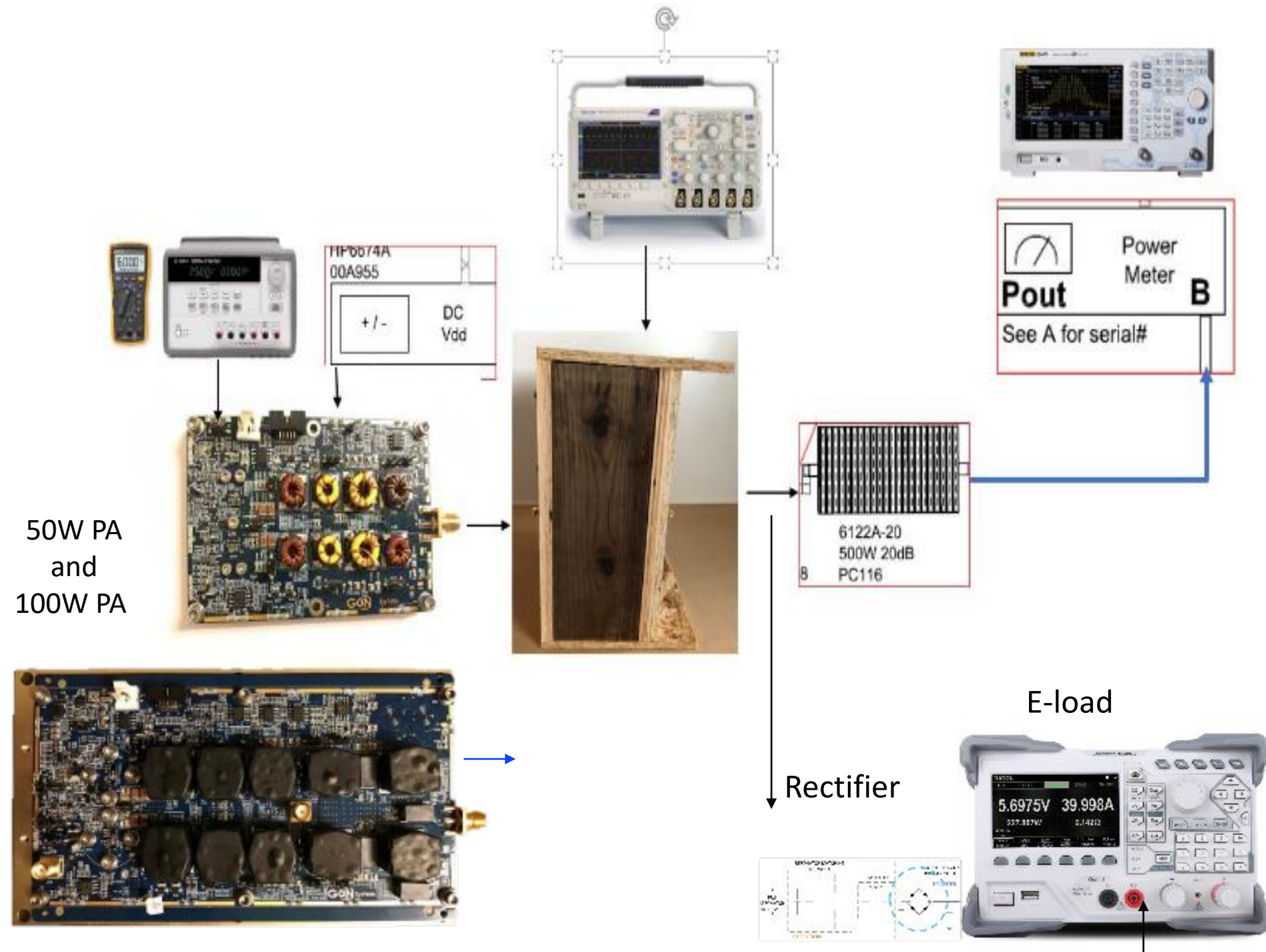- System test setup for performance tests
- End to End measurement with 50 ohm system
- End to End system tests performed with electronic load
- Two PAs tested for 25W and 50W Rx power





Conditions

- 50W PA
- 200mm air gap
- 50 ohm load, no rectifier

Results

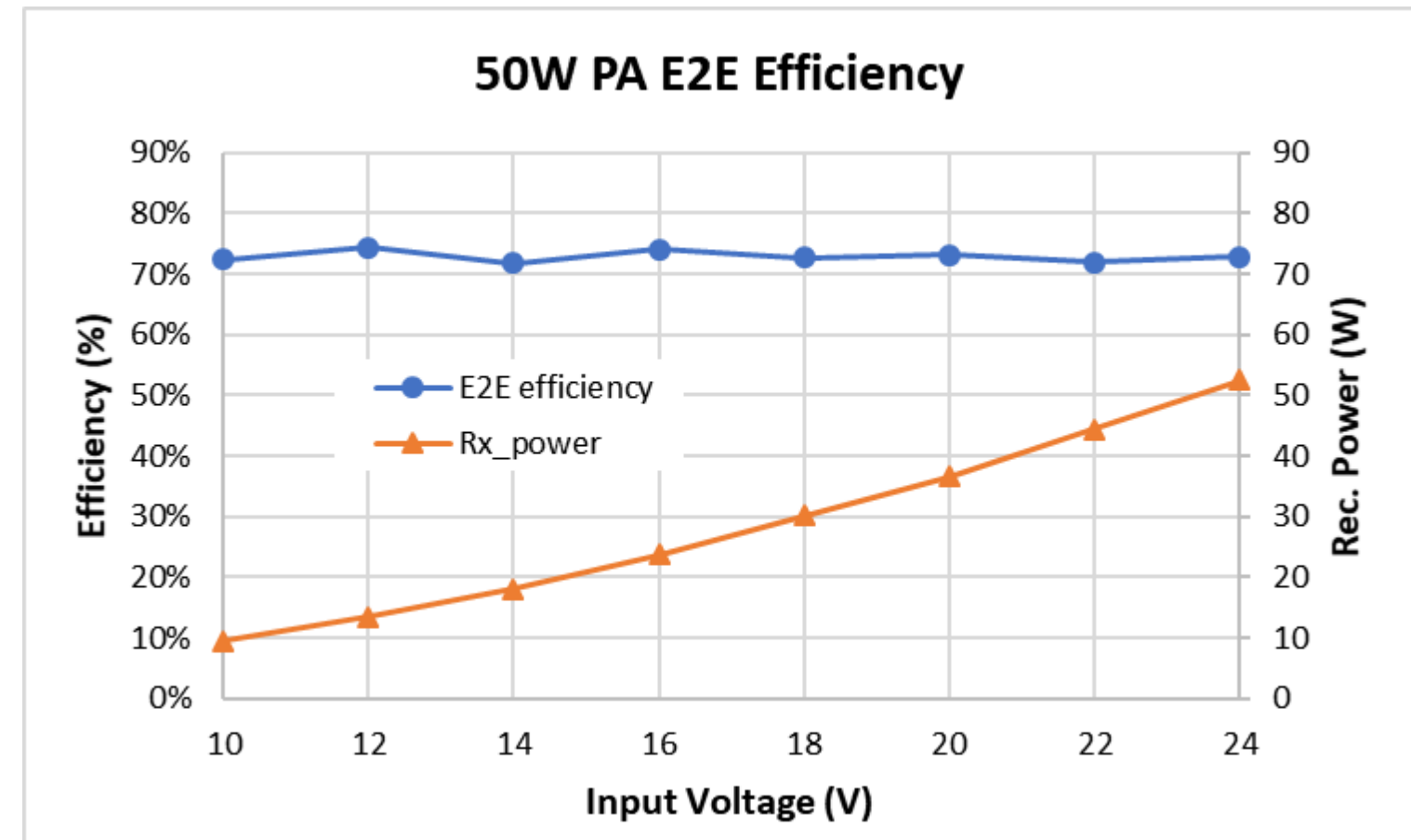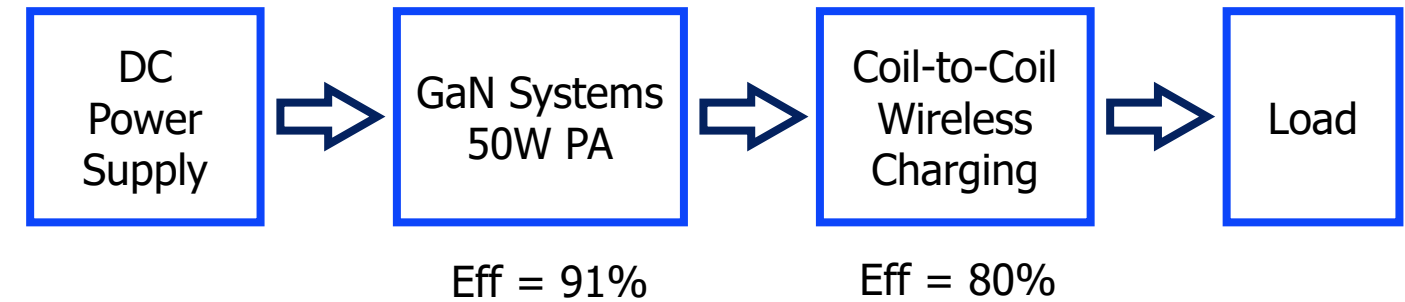- PA efficiency: 91%
- Coil to coil efficiency: 80%
- End to end efficiency: 72%





Conditions

- 50W PA
- 200mm air gap
- Rectifier in system
- Sweep 60-140 ohm @25V

Results

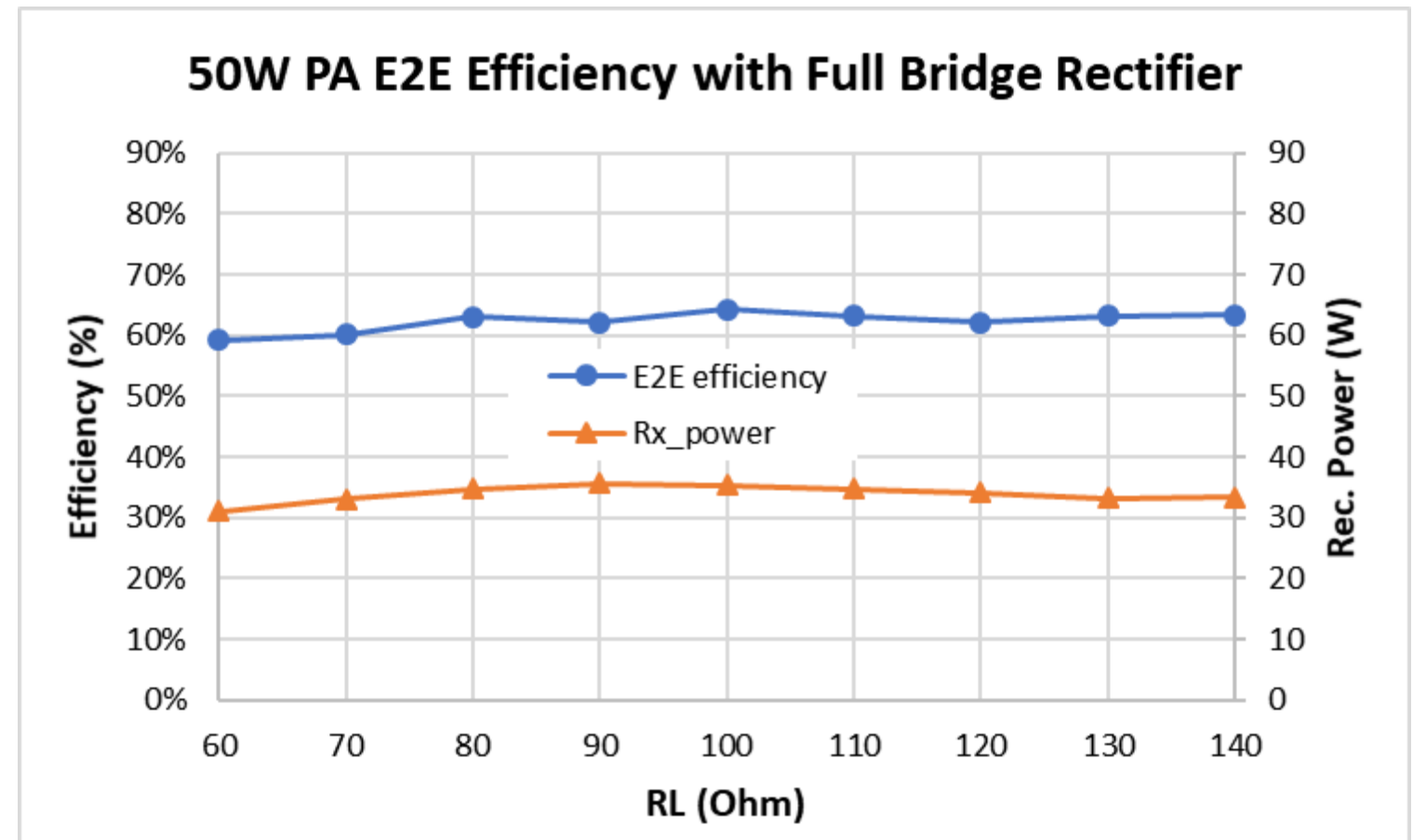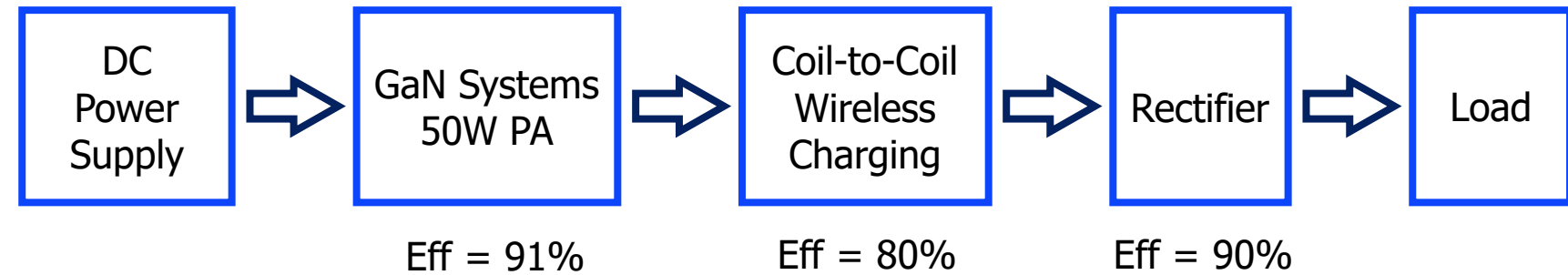- PA efficiency: 91%
- Coil to coil efficiency: 80%
- Rectifier efficiency: 90%
- End to end efficiency: 63%





Conditions

- 100W PA
- 200mm air gap
- 50 ohm load, no rectifier

Results

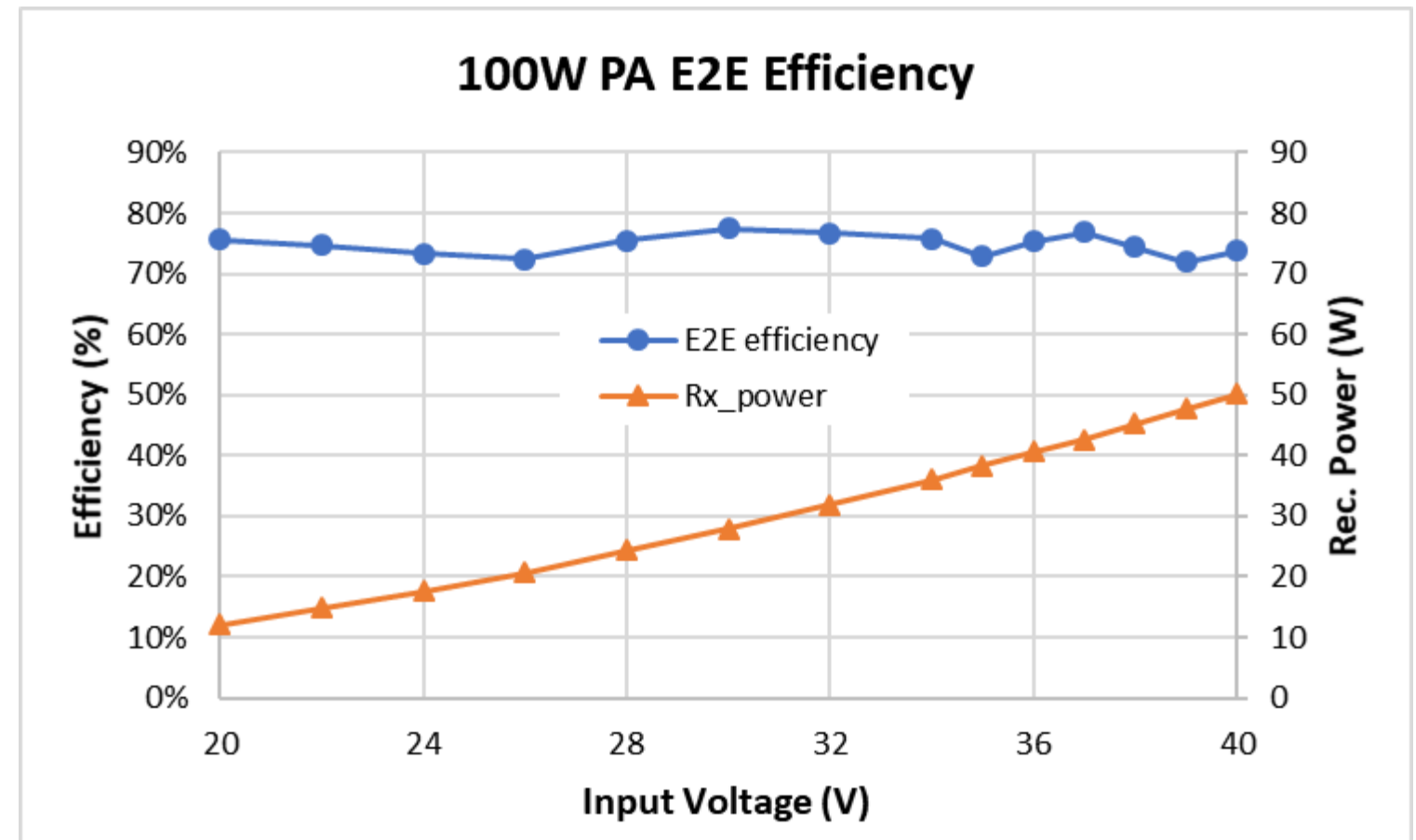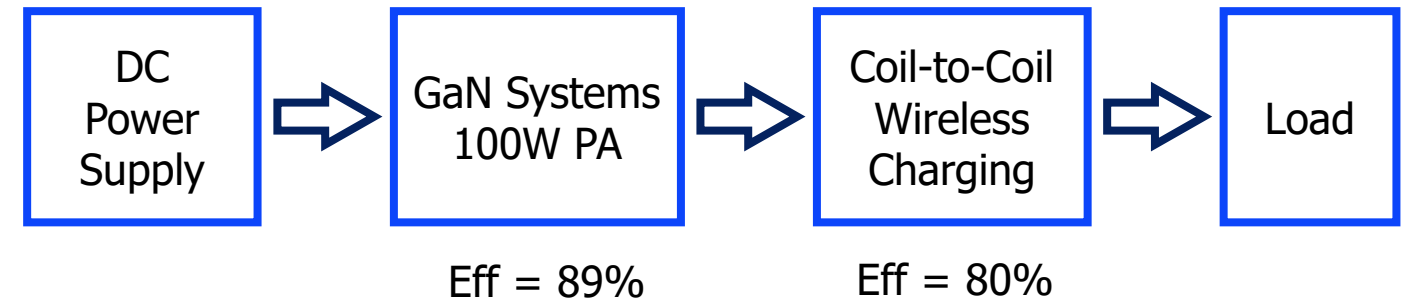- PA efficiency: 89%
- Coil to coil efficiency: 80%
- End to end efficiency: 75%





Conditions

- 100W PA
- 200mm air gap
- Rectifier in system
- Sweep 60-140 ohm @29V

Results

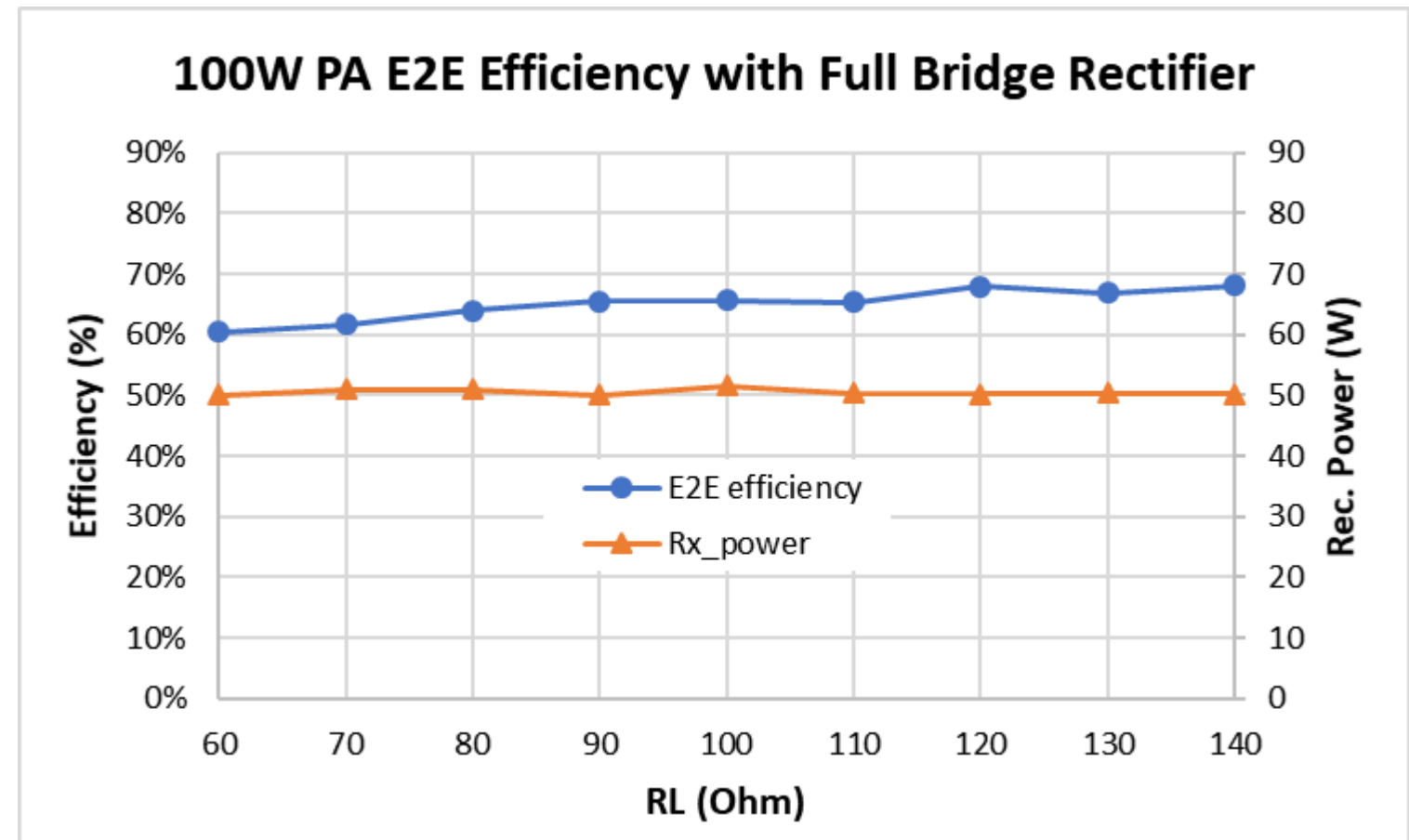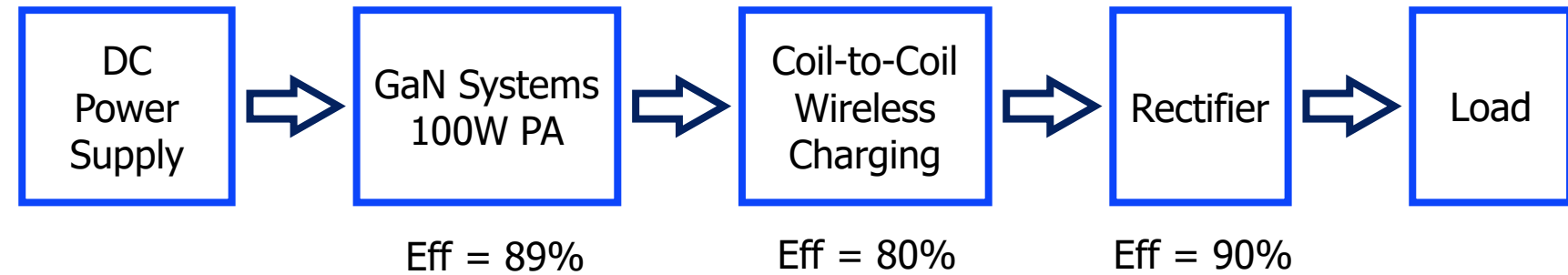- PA efficiency: 89%
- Coil to coil efficiency: 80%
- Rectifier efficiency: 90%
- End to end efficiency: 68%



- Seeing more and more applications
 - Industrial, Consumer, Medical
- Application requirements
 - High Tx power (50W to 1000W)
 - Spatial freedom
 - Large coil-to-coil gap
- Achieve excellent performance with GaN Systems devices
 - High efficiency
 - Good EMI
 - Low thermals

